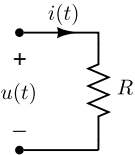


$$u(t) = \sqrt{2}U \cos(\omega t + \varphi_u) = \Re[\sqrt{2}e^{j\omega t}\mathcal{U}]$$

$$i(t) = \sqrt{2}I \cos(\omega t + \varphi_i) = \Re[\sqrt{2}e^{j\omega t}\mathcal{I}]$$




$$u(t) = R \cdot i(t)$$



$$\Re[\sqrt{2}e^{j\omega t}\mathcal{U}] = \Re[\sqrt{2}e^{j\omega t}R\mathcal{I}]$$



$$\Re[\sqrt{2}e^{j\omega t} \{\mathcal{U} - R \cdot \mathcal{I}\}] = 0$$
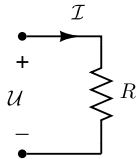
$$\Rightarrow$$


$$\mathcal{U} = R \cdot \mathcal{I}$$